

Question 8

Answer saved

Marked out of
4

Flag
question

Match the truth table with the logic gate

NAND =

X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

NOR =

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0

XOR

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0

XNOR =

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	1

When simplified with Boolean Algebra $(x + y)(x + z)$ simplifies to

Select one:

☐ a. $x + x(y + z)$

☐ b. x

☐ c. $x(1 + yz)$

☐ d. $x + yz$

For the hexadecimal number A9F7, the weight of the column with the 9 is

- ☐ a. 4096
- ☐ b. 1
- ☐ c. 16
- ☒ d. 256

[Clear my choice](#)

Assume that a floating point number is represented in binary. If the sign bit is 0, the

- ☐ a. number is negative
- ☐ b. exponent is positive
- ☒ c. exponent is negative
- ☐ d. number is positive

[Clear my choice](#)

Clear my choice

Question **16**

Answer saved

Marked out of 1

🚩 Flag question

1's complement representation of decimal number of -17 by using 8 bit representation is

Select one:

- ☐ a. 1101 1101
- ☒ b. 0001 0001
- ☐ c. 1100 1100
- ☐ d. 1110 1110

Clear my choice

Previous page

Next page

The minimum expression that can be read from the Karnaugh map shown is

	\bar{C}	C
$\bar{A}\bar{B}$	1	1
$\bar{A}B$		
AB		
$A\bar{B}$	1	1

Select one:

- ☐ a. $X = \bar{A}$
- ☐ b. $X = A$
- ☒ c. $X = \bar{B}$
- ☐ d. $X = B$

Clear my choice

Which of the following expressions is in the product-of-sums form?

Select one:

- ☒ a. $AB + CD$
- ☐ b. $(A + B)(C + D)$
- ☐ c. $AB(CD)$
- ☐ d. $(AB)(CD)$


[Clear my choice](#)

Match the two level gate networks and logical expressions with their diagrams


Sum-of-Products (SOP) logical expressions

$$A \cdot B + A \cdot C' + B \cdot C' + A + C$$

Two level AND-OR Networks

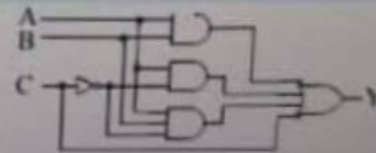

Two level OR-AND Networks

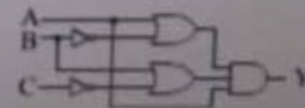

Question 7

Not yet
answered

Marked out of
1

Flag
question

The simplification of the Boolean $(\overline{A}BC) + (A\overline{B}C)$ expression is

Select one:

- ☐ a. A
- ☐ b. 0
- ☐ c. BC
- ☐ d. 1


Question 5

Answer saved

Marked out of

Flag
Question

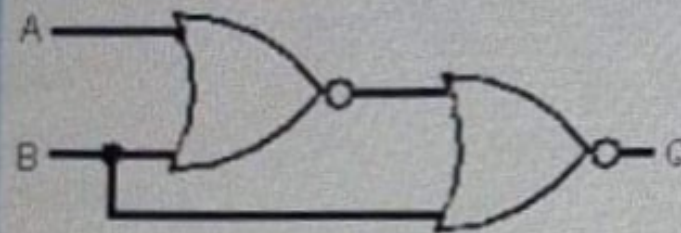Complete the truth table for the given diagram



A	B	Q
0	0	
0	1	
1	0	
1	1	

	A	B	Q
--	---	---	---

0

0

1

0

For the hexadecimal number A9F7, the weight of the column with the 9 is

256

a ☐

4096

b ☐

1

c ☒

16

d ☐

أدخل اختياري

- إنهاء المحاولة

Next activity

→ Slides



الانتقال إلى...

الزيود

Question 9

Not yet answered

Marked out of 1

Flag question

Assume that a floating point number is represented in binary. If the sign bit is 0, the

- ☐ a. exponent is negative
- ☐ b. number is positive
- ☐ c. exponent is positive
- ☐ d. number is negative

The weight for the digit 5 in the octet number 1 4 5 7 6


- ☐ a. 5
- ☒ b. 64
- ☐ c. 8
- ☐ d. 256

[Clear my choice](#)

Question **6**

Answer saved

Marked out of 1

 Flag question

For the oct number 5735, the weight of the column with the **3** is

- ☒ a. 64
- ☐ b. 1

Question 1

Answer saved

Marked out of 1

Flag question

Which of the following is not a basic Boolean operation?

Select one:

- ☐ a. NAND
- ☐ b. AND
- ☐ c. NOR
- ☒ d. FOR

Clear my choice

البوابة التعليمية الإلكترونية لجامعة الإسراء

Clear my choice

The weight for the digit 5 in the octet number 1 4 5 7 6

- ☐ a. 5
- ☐ b. 64
- ☐ c. 8
- ☐ d. 256

4
The 1's complement representation of decimal number of -17 by using 8 bit

Select one:

- ☒ a. 0001 0001
- ☐ b. 1101 1101
- ☐ c. 1100 1100
- ☐ d. 1110 1110

The simplification of the Boolean $(\overline{A}BC) + (A\overline{B}C)$ expression is

Select one:

- ☐ a. BC
- ☒ b. 1
- ☐ c. A
- ☐ d. 0

Clear my choice

If we use the Boolean algebra rules to simplify the function $f = x'y + xy + y$, then the result will be:

- ☒ a. y
- ☐ b. x
- ☐ c. x + y
- ☐ d. xy

Clear my choice

Adjacent cells of a Karnaugh map
d/quiz/attempt.php?attempt=51245&cmid=75815&page=3

Maps

البوابة التعليمية الإلكترونية لجامعة

Clear my choice

When simplified with Boolean Algebra $(x + y)(x + z)$ simplifies to

Select one:

- ☐ a. $x + x(y + z)$
- ☒ b. $x + yz$
- ☐ c. $x(1 + yz)$
- ☐ d. x

Clear my choice

سؤال 6

لم يتم الإجابة عليه بعد

الدرجة من 1

علم هذا السؤال

The decimal equivalent of hex number
1A52 is

اختر أحد الخيارات

a. 6379 ☐

b. 6738 ☒

c. 6793 ☐

d. 6973 ☐

Next page

Previous page



Logic Design

الصفحة الرئيسية / مقرراتي الدراسية / Logic Design / Final Exam_Logic Design_2020 / Topic 1 /

سؤال 21

لم يتم الاجابة عليه بعد

الدرجة من 2

علم هذا السؤال

Boolean $(\overline{A}B\overline{C}) + (\overline{A}\overline{B}C)$ expression is

اختر أحد الخيارات

a. 0 ☐

b. A ☐

c. BC ☐

d. 1 ☐

سؤال 22

اختر أحد الخيارات

a. $F(A,B,C,D) = S$ ☒

((1,3,4,5,6,7,9,12,14

b. $F(A,B,C,D) = S$ ☐

((1,3,4,5,6,7,9,10,13

c. $F(A,B,C,D) = S$ ☐

((1,3,4,5,6,7,8,12,13

d. $F(A,B,C,D) = S$ ☐

((1,3,4,5,6,7,9,12,13

لم يتم الإجابة عليه بعد

الدرجة من 2

علم هذا السؤال 

?Why latches are called a memory devices

اختر أحد الخيارات

- a. It can store one bit of data ☐
- b. It can store infinite amount of ☐
data
- c. It has internal memory of 4 bit ☐
- d. It has capability to store 8 bits of ☐
data

A full adder logic circuit will have

اختر أحد الخيارات

- a. Three inputs and three outputs ☒
- b. Two inputs and one output ☐
- c. Two inputs and two outputs ☐
- d. Three inputs and two outputs ☐

Next page

Previous page

سؤال 3

لم يتم الإجابة عليه بعد

الدرجة من 1

علم هذا السؤال 

What is the binary equivalent of the decimal number **465**

اختر أحد الخيارات

a. 101110000 ☐

b. 111010001 ☒

c. 110110000 ☐

d. 111100000 ☐

Next page

Previous page

?_____ The SR latch consists of

اختر أحد الخيارات

a. 4 inputs ☐

b. 1 input ☐

c. 2 inputs ☒

d. 3 inputs ☐

سؤال 2

تم حفظ الإجابة

الدرجة من 2

علم هذا السؤال 

Convert the binary number 1001.0010_2 to decimal

The simplification of the Boolean $(\overline{A}BC) + (A\overline{B}C)$ expression is

Select one:

- ☒ a. 1
- ☐ b. 0
- ☐ c. BC
- ☐ d. A

Clear my choice

If we use the Boolean algebra rules to simplify the function $f = x'y + xy + y$, then the result will be:

سؤال 3

لم يتم الإجابة عليه بعد

الدرجة من 1

علم هذا السؤال 

What is the binary equivalent of the decimal number **465**

اختر أحد الخيارات

a. 101110000 ☐

b. 111010001 ☒

c. 110110000 ☐

d. 111100000 ☐


Next page

Previous page

Question 2

Not yet answered

Marked out of 2

 Flag question

Which one of the following expressions determines whether the value of the `length` variable is greater than or equal to the value of the `width` variable?

Select one:

- ☐ a. `length >= width`
- ☐ b. `length > width`
- ☐ c. `length < width`
- ☐ d. `width <= length`

1's complement representation of decimal number of -17 by using 8 bit representation is

Select one:

- ☒ a. 1110 1110
- ☐ b. 1100 1100
- ☐ c. 1101 1101
- ☐ d. 0001 0001

The SR latch consists of _____?

Select one:

- ☒ a. 2 inputs
- ☐ b. 1 input
- ☐ c. 3 inputs
- ☐ d. 4 inputs

Question 14

Not yet
answered
Marked out ofFlag
question

$$(734)_8 = (\quad)_{16}$$

Select one:

- ☐ a. DC1
- ☒ b. 1DC
- ☐ c. C1D
- ☐ d. 1CD


Question 15

Not yet
answered
Marked out ofFlag
question

What is the binary equivalent of the decimal number 465

Select one:

- ☐ a. 110110000
- ☒ b. 111010001
- ☐ c. 101110000
- ☐ d. 100010111

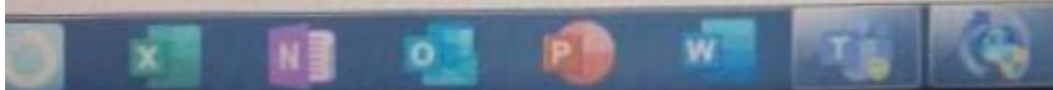[Previous page](#)

DELL

The full form of SR is _____?

Select one:

- ☐ a. Set Rated
- ☒ b. Set reset
- ☐ c. Set ready
- ☐ d. System rated

Latch is a device with _____?

Select one:

- ☐ a. Three stable state
- ☐ b. Infinite stable states
- ☐ c. One stable state
- ☒ d. Two stable state

Which of following are known as universal gates

Select one:

- ☐ a. AND & OR
- ☒ b. NAND & NOR
- ☐ c. XOR & OR
- ☐ d. None

The full form of SR is _____?

Select one:


Question 22

Not yet
answered

Marked out of 2

Flag
question

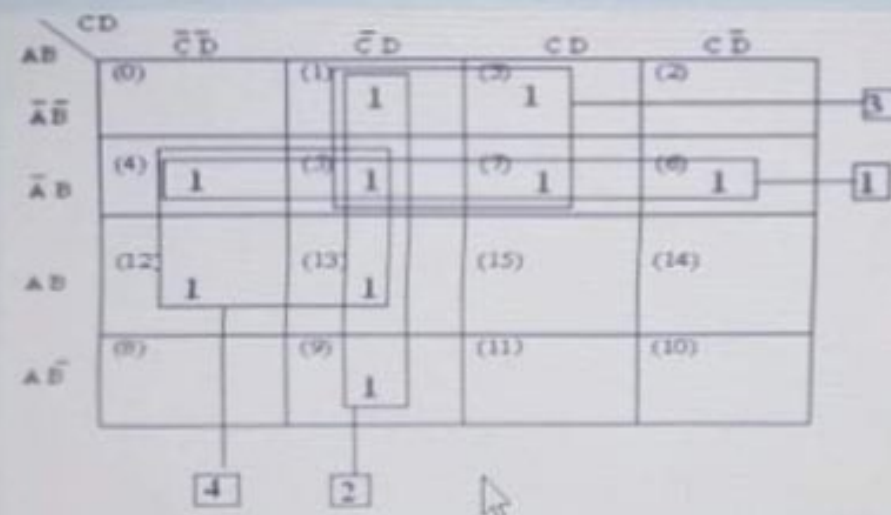The K-Map shown below is representing the function:



Select one:

- ☐ a. $F(A,B,C,D) = \sum (1,3,4,5,6,7,9,12,14)$
- ☐ b. $F(A,B,C,D) = \sum (1,3,4,5,6,7,9,10,13)$
- ☒ c. $F(A,B,C,D) = \sum (1,3,4,5,6,7,9,12,13)$
- ☐ d. $F(A,B,C,D) = \sum (1,3,4,5,6,7,8,12,13)$

☐ c. 8

☐ d. 16

Question 20

Not yet
answered

Marked out of 2

Flag
question

The output of an exclusive-NOR gate is HIGH if _____

Select one:

- ☒ a. None of the above
- ☐ b. The inputs are equal
- ☐ c. The inputs are not equal Gate
- ☐ d. One input is HIGH, and the other input is LOW.

Previous page



Next page

Why latches are called a memory devices?

Select one:

- ☒ a. It can store one bit of data
- ☐ b. It has internal memory of 4 bit
- ☐ c. It has capability to store 8 bits of data
- ☐ d. It can store infinite amount of data

The K-Map shown below is representing the function

Question 18

Not yet
answered

Marked out of 2

Flag
question

The basic properties of Boolean algebra are:

Select one:

- ☐ a. Commutative Property
- ☐ b. Associative Property
- ☒ c. All the answers are true
- ☐ d. Distributive Property

Question 19

Not yet
answered

Marked out of 2

Remove flag

How many entries would a truth table for a four input NAND gate have?

Select one:

- ☐ a. 2
- ☒ b. 4
- ☐ c. 8
- ☐ d. 16

Question 16

Not yet answered

Marked out of 2

Flag question

The fractional binary number 0.11 has a decimal value of

Select one:

- ☐ a. $\frac{1}{4}$
- ☐ b. 1
- ☐ c. $\frac{3}{4}$
- ☒ d. $\frac{3}{8}$

Question 17

Not yet answered

Marked out of 2

Flag question

The number 1010 in BCD is

Select one:

- ☐ a. invalid
- ☒ b. equal to decimal ten
- ☐ c. equal to decimal eight
- ☐ d. equal to decimal twelve

QUIZ NAVIGATION

العدد الصحيح المثلث

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15
16	17	18	19	20
21	22	23	24	25

Final answer

Time left 0:36:26

Question 12

Not yet answered

Marked out of 2

Flag question

When an input signal $A=11001$ is applied to a NOT gate serially, its output signal is

Select one:

- ☐ a. 10101
- ☒ b. 00110
- ☐ c. 00111
- ☐ d. 11001

Question 13

Not yet answered

Marked out of 2

Flag question

The Boolean expression $A + 1$ is equal to

Select one:

- ☒ a. 1
- ☐ b. A
- ☐ c. 0
- ☐ d. AA

Question 14

Not yet answered

Output will be a LOW for any case when one or more inputs are zero for an

21	22	23	24	25

Flash attempt

Time left 0:40:54

Question 14

Not yet
answered

Marked out of 2

Flag
question

Output will be a LOW for any case when one or more inputs are zero for a(n)

Select one:

- ☐ a. OR Gate
- ☒ b. AND Gate
- ☐ c. XOR Gate
- ☐ d. NAND Gate

Question 15

Not yet
answered

Marked out of 2

Flag
questionThe Boolean $\bar{A}B + A\bar{B} + AB$ expression is equivalent to

Select one:

- ☐ a. AB
- ☐ b. $A+B$
- ☒ c. $A+B$
- ☐ d. $A(B)$

[Previous page](#)[Next page](#)

Question 10

Not yet
answered

Marked out of 2

Flag
question

Convert the binary number $1001\ 0010_2$ to decimal

Select one:

- ☐ a. 125
- ☐ b. 90.125
- ☒ c. 9.125
- ☐ d. 9.5

[Previous page](#)

[Next page](#)

Question 9

Not yet
answered

Marked out of 2

Flag
question

The minimum expression that can be read from the Karnaugh map shown is

	\bar{C}	C
$\bar{A}\bar{B}$		
$\bar{A}B$		
AB	1	1
$A\bar{B}$	1	1

Select one:

- ☒ a. $X=A$
- ☐ b. \bar{A}
- ☐ c. $X=\bar{B}$
- ☐ d. $X=B$

Question 6

Not yet
answered

Marked out of 2

Flag
question

A full adder logic circuit will have

Select one:

- ☒ a. Three inputs and two outputs
- ☐ b. Three inputs and three outputs
- ☐ c. Two inputs and two outputs
- ☐ d. Two inputs and one output

Question 7

Not yet
answered

Marked out of 2

Flag
question

The code where all successive numbers differ from their preceding number by single bit is

Select one:

- ☒ a. Binary code
- ☐ b. BCD
- ☐ c. Gray
- ☐ d. Excess - 3

QUIZ NAVIGATION

أحمد العرعر

1	2	3	4
5	6	7	8
9	10	11	12
13	14	15	16
17	18	19	20
21	22	23	24

Finish attempt

Time left 0:46:26

Question

- ☐ b. BCD
- ☐ c. Gray
- ☐ d. Excess - 3

Question 8

Not yet
answered

Marked out of 2

Flag
question

The basic logic gate whose output is the complement of the input is the:

Select one:

- ☐ a. OR Gate
- ☐ b. AND Gate
- ☐ c. Comparator
- ☒ d. Inverter

Question 9

Not yet
answered

The minimum expression that can be read from the Karnaugh map shown is

The 2's complement of the number 1101110 is

Select one:

- ☐ a. 0010001
- ☐ b. 0010001
- ☐ c. None
- ☒ d. 0010010

Design

Plans

5

Topic 1

Quizzes &
Exams

Topic 9

Topic 10

Topic 11

Topic 12

Topic 13

Topic 14

Question 3

Not yet
answered

Marked out of 2

Flag
question

The following switching functions are to be implemented using a Decoder

$$f_1 = \sum m(1, 2, 4, 8, 10, 14) \quad f_2 = \sum m(2, 5, 9, 11) \quad f_3 = \sum m(2, 4, 5, 6, 7)$$

The minimum configuration of the decoder should be

Select one:

- ☒ a. 3-to-8 line
- ☐ b. 2-to-4 line
- ☐ c. 4-to-16 line
- ☐ d. 5-to-32 line

Question 4

Not yet
answered

Marked out of 2

Flag
question

Which of the following gate will give a 0 when both of its inputs are 1?

Select one:

- ☐ a. EXOR
- ☐ b. OR
- ☐ c. AND
- ☒ d. NAND

ants

Topic 1

Quizzes &
Exams

Topic 9

Topic 10

Topic 11

Topic 12

Topic 13

Topic 14

Question 1

Not yet
answered

Marked out of 2

Flag
question

How many AND gates are required to realize $Y = CD + EF + G$

Select one:

- ☒ a. 2
- ☐ b. 4
- ☐ c. 3
- ☐ d. 5

Question 2

Not yet
answered

Marked out of 2

Flag
question

Which of the following logical operations is represented by the $+$ sign in Boolean algebra?

Select one:

- ☒ a. OR Gate
- ☐ b. Comparator
- ☐ c. AND Gate
- ☐ d. Inverter

QUIZ NAVIGATION

برسید احمد البرعش

1	2	3	4
6	7	8	9
11	12	13	14
16	17	18	19
21	22	23	24

Finish attempt

Time left 0:48:10

- ☐ d. an OR or an EX-NOR

25

d
out of 2

A counter circuit is usually constructed of _____

Select one:

- ☐ a. A number of latches connected in cascade form
- ☒ b. A number of flip-flops connected in cascade
- ☐ c. A number of NAND gates connected in cascade form
- ☐ d. A number of NOR gates connected in cascade form

vious page

Finish attempt

If a signal passing through a gate is inhibited by sending a LOW into one of the inputs, and the output is HIGH, the gate is a(n)

Select one:

- ☐ a. NOR
- ☐ b. AND
- ☒ c. NAND
- ☐ d. OR

The output of a logic gate is 1 when all its inputs are at logic 0 the gate is either

Logic Design

Home / My courses / Logic Design / Topic 8 / Assignment Logic Design_2020

Question 1

Not yet answered

Marked out of 2

Flag question

When simplified with Boolean Algebra $(x + y)(x + z)$ simplifies to

Select one:

- ☒ a. $x + yz$
- ☐ b. x
- ☐ c. $x + x(y + z)$
- ☐ d. $x(1 + yz)$

Question 2

Not yet answered

Marked out of 2

Flag question

Which of the following logical operations is represented by the $+$ sign in Boolean algebra?

Select one:

- ☒ a. OR Gate
- ☐ b. Inverter
- ☐ c. Comparator
- ☐ d. AND Gate

- ☐ b. AND
- ☒ c. NAND
- ☐ d. OR

Question 24

Not yet

answered

Marked out of 2

Flag

Question

The output of a logic gate is 1 when all its inputs are at logic 0. the gate is either

Select one:

- ☒ a. a NOR or an EX-NOR
- ☐ b. an AND or an EX-OR
- ☐ c. a NAND or an EX-OR
- ☐ d. an OR or an EX-NOR

Question 25

Not yet

A counter circuit is usually constructed of _____

The chief reason why digital computers use complemented subtraction is that it

Select one:

- ☒ a. Can handle negative numbers easily
- ☐ b. Avoids direct subtraction
- ☐ c. Simplifies the circuitry
- ☐ d. Is a very simple process

Question 6

yet
covered
ked out of

lag
tion

The number 1010 in BCD is

Select one:

- ☐ a. invalid
- ☐ b. equal to decimal eight
- ☒ c. equal to decimal ten
- ☐ d. equal to decimal twelve

Question 7

et
ered
ed out of

g
ion

How many two-input AND and OR gates are required to realize $Y = CD + EF + G$

Select one:

- ☐ a. 2,3
- ☒ b. 2,2
- ☐ c. none of these
- ☐ d. 3,3

Question 8

t
red

How many select lines will a 32:1 multiplexer will have

Select one:



How many select lines will a 32:1 multiplexer will have

Select one:

- ☐ a. 11
- ☐ b. 8
- ☒ c. 5
- ☐ d. 9

- ☐ c. Comparator
- ☐ d. AND Gate

Question 3

Not yet answered

Marked out of 2

Flag question

The hexadecimal number 'A1' has the decimal value equivalent to

Select one:

- ☐ a. 100
- ☐ b. 80
- ☒ c. 161
- ☐ d. 256

Question 4

Not yet answered

Marked out of 2

Flag question

The decimal equivalent of Binary number 11011 is

Select one:

- ☐ a. 26
- ☐ b. 36
- ☒ c. 27
- ☐ d. 16

Question 5



Which is the major functioning responsibility of the multiplexing combinational circuit?

Select one:

- ☐ a. Decoding the binary information
- ☐ b. Encoding of binary information
- ☐ c. Generation of all minterms in an output function with OR-gate
- ☒ d. Generation of selected path between multiple sources and a single destination